


Week 2, Reducing circuits using Boolean algebra




Which is Better?

- Which implementation do you prefer? Why?

A.

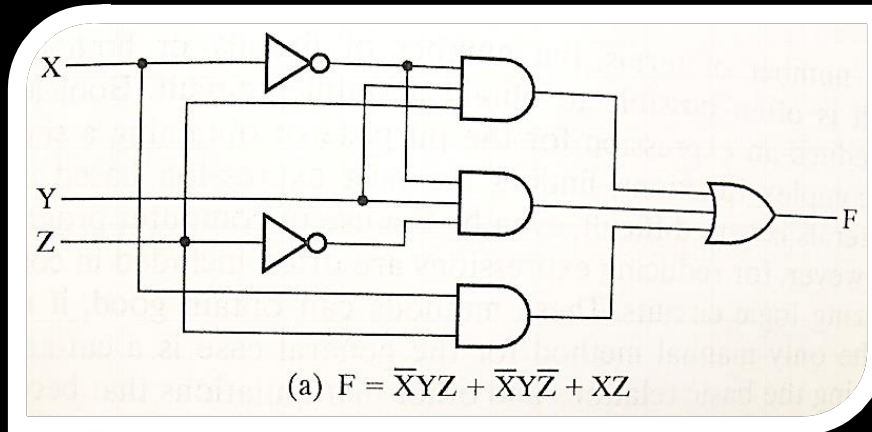

B.

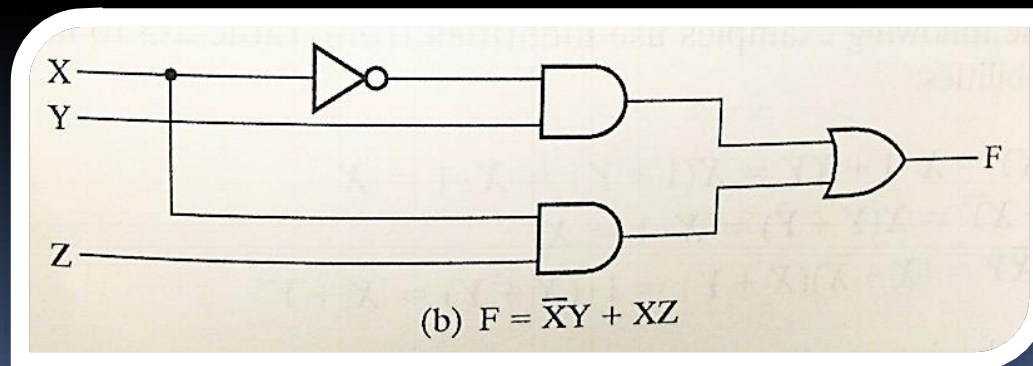


Remember this circuit?


- We previously built this circuit using SOM
- Can we simplify it?

$$m_0 + m_1 + m_2 + m_3 =$$
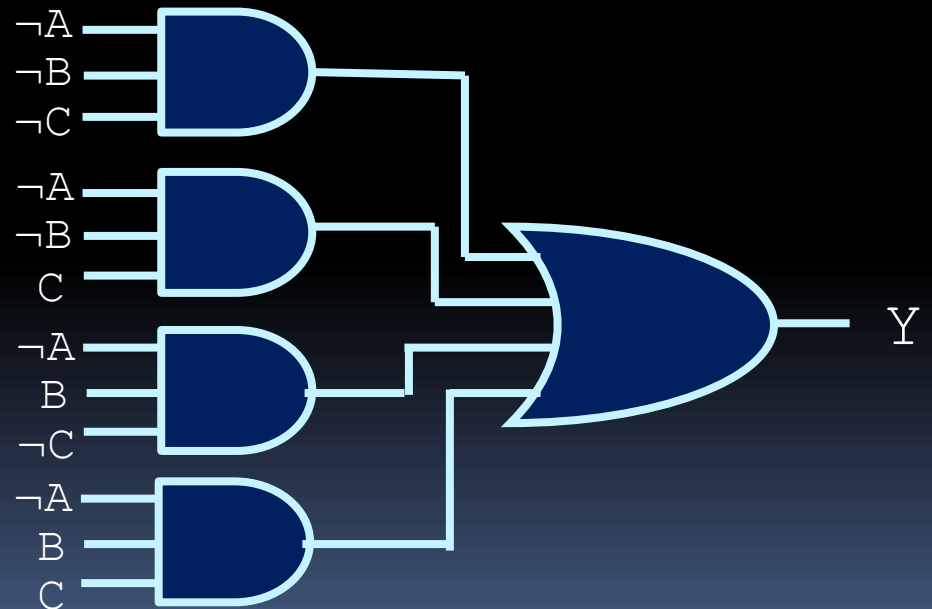
$$\overline{A} \cdot \overline{B} \cdot \overline{C} + \overline{A} \cdot \overline{B} \cdot C + \overline{A} \cdot B \cdot \overline{C} + \overline{A} \cdot B \cdot C =$$



Reasons for reducing circuits

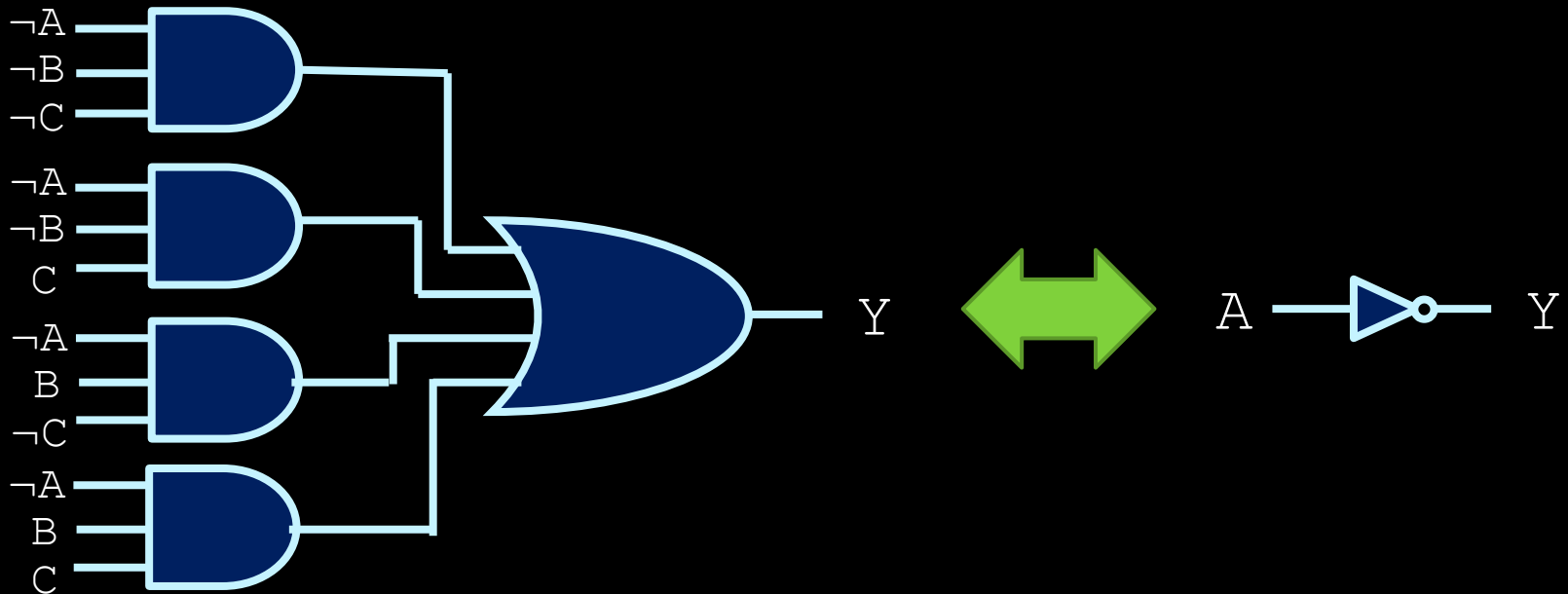

- To minimize the number of gates, we want to reduce the boolean expression as much as possible from a collection of minterms to something smaller.
- This is where CSCA67 skills come in handy 😊

Boolean algebra review

- Axioms:

$$0 \cdot 0 = 0$$

$$1 \cdot 1 = 1$$

$$0 \cdot 1 = 1 \cdot 0 = 0$$

$$\text{if } x = 1, \overline{x} = 0$$

- From this, we can extrapolate:

If one input of a 2-input AND gate is 1, then the output is whatever value the other input is.

$$x \cdot 0 =$$

$$x \cdot 1 =$$

$$x \cdot x =$$

$$x \cdot \overline{x} =$$

$$\overline{\overline{x}} =$$

$$x + 1 =$$

$$x + 0 =$$

$$x + x =$$

$$x + \overline{x} =$$

If one input of a 2-input OR gate is 0, then the output is whatever value the other input is.

Boolean identities

- Commutative Law:

$$x \cdot y = y \cdot x \qquad x + y = y + x$$

- Associative Law:

$$\begin{aligned} x \cdot (y \cdot z) &= (x \cdot y) \cdot z \\ x + (y + z) &= (x + y) + z \end{aligned}$$

- Distributive Law:

$$\begin{aligned} x \cdot (y + z) &= x \cdot y + x \cdot z \\ x + (y \cdot z) &= (x + y) \cdot (x + z) \end{aligned}$$

Does this hold in conventional algebra?

Boolean identities


- Simplification Law:

$$x + (\bar{x} \cdot y) = x + y \qquad x \cdot (\bar{x} + y) = x \cdot y$$

- Consensus Law:

$$x \cdot y + \bar{x} \cdot z + y \cdot z = x \cdot y + \bar{x} \cdot z$$

- Proof by Venn diagram:

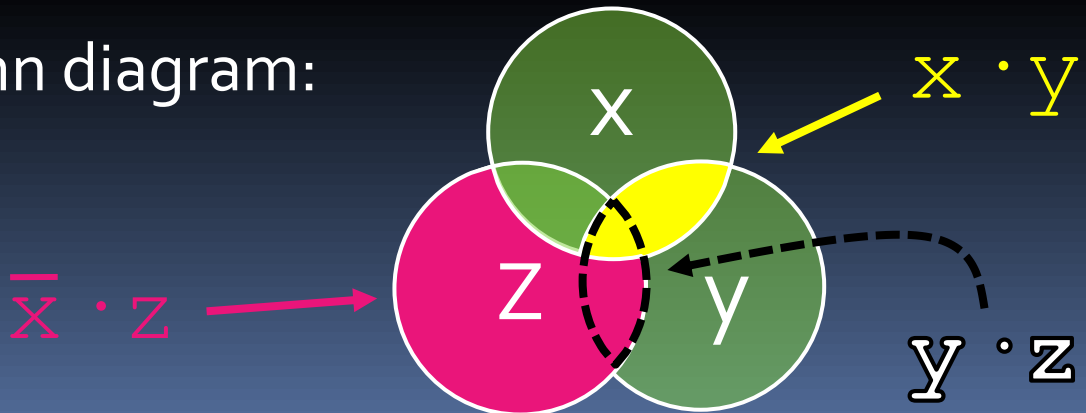

Boolean identities

- Absorption Law:

$$x \cdot (x + y) = x$$

$$x + (x \cdot y) = x$$

- De Morgan's Laws:

$$\overline{x} \cdot \overline{y} = \overline{x + y}$$

$$\overline{x + y} = \overline{x} \cdot \overline{y}$$




Converting to NAND gates

- De Morgan's Law is important because out of all the gates, NANDs are the cheapest to fabricate.
 - Can convert a Sum-of-Minterms (also known as sum-of-products) circuit to an equivalent circuit of NAND gates:




Converting SOM to NAND gates

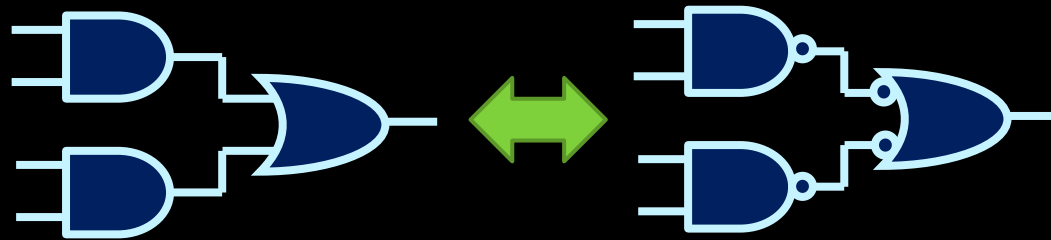- Start by adding two NOT gates on internal wires. Recall that $x = \sim(\sim x)$



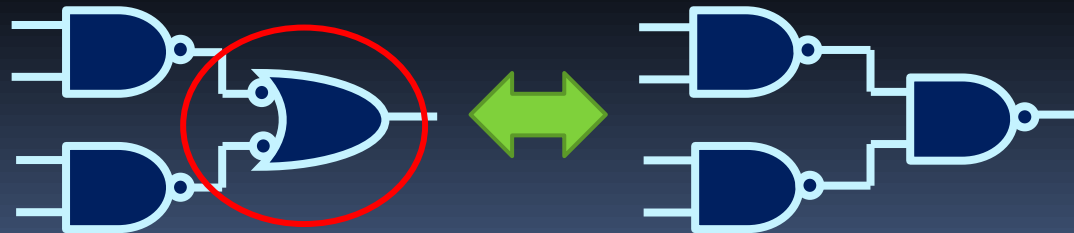- Apply de Morgan's law to the final or gate:
 $\overline{x} + \overline{y} = \overline{x \cdot y} = \text{NAND}(x, y)$



Reducing Boolean expressions

A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

- Using SOM:

$$Y = \bar{A} \cdot B \cdot C + A \cdot \bar{B} \cdot \bar{C} + \boxed{A \cdot B \cdot \bar{C}} + \boxed{A \cdot B \cdot C}$$

- Now start combining terms, like the last two:

$$Y = \bar{A} \cdot B \cdot C + A \cdot \bar{B} \cdot \bar{C} + \boxed{A \cdot B}$$

Reducing Boolean expressions

- Different final expressions possible, depending on what terms you combine.
- For instance, given the previous example:

$$Y = \bar{A} \cdot B \cdot C + A \bar{B} \bar{C} + A \cdot B \cdot \bar{C} + A \cdot B \cdot C$$


- If you combine the end and middle terms...

$$Y = B \cdot C + A \cdot \bar{C}$$

- Which reduces the number of gates and inputs!

Reducing Boolean expressions

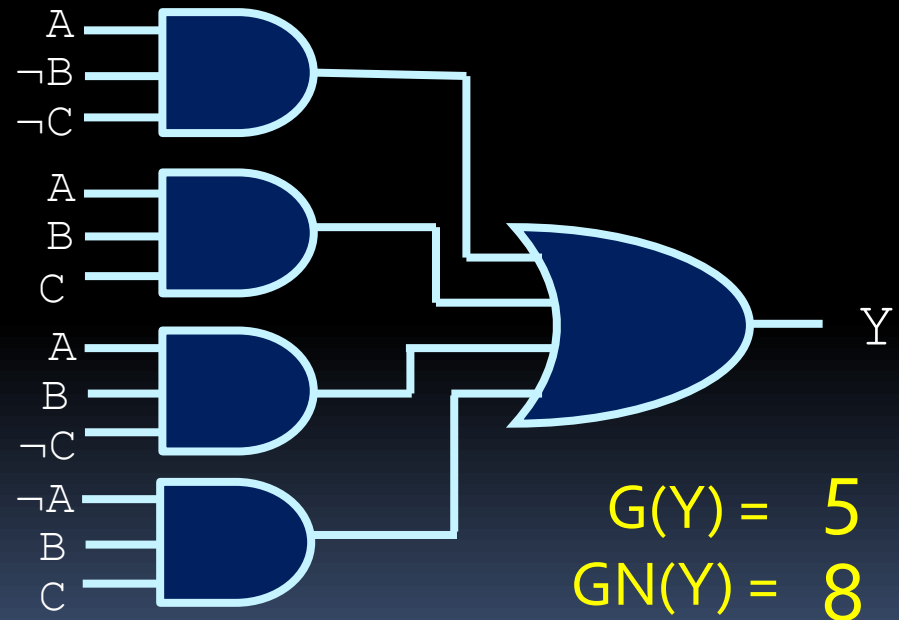- What is considered the “simplest” expression?
 - In this case, “simple” denotes the lowest **gate cost** (G) or the lowest **gate cost with NOTs** (GN).
 - To calculate the gate cost, simply add all the gates together (as well as the cost of the NOT gates, in the case of the GN cost).
 - In this example the cost per gate is 1



Don't count $\neg C$ twice!

Algebraic Intuition?

- We don't like the fact that we need to rely on "intuition" to reduce using algebra.
 - What if we miss a step?
- Is there a simpler process that is repeatable?
- Next up, Karnaugh maps!

Karnaugh maps

0	0	1	1
0	0	1	1
0	0	0	1
0	1	1	1

Reducing Boolean expressions

- How do we find the “simplest” expression for a circuit?
 - Technique called **Karnaugh maps** (or K-maps).
 - Karnaugh maps are a 2D grid of minterms, where adjacent minterm locations in the grid **differ by a single input** (literal).
 - Values of the grid are the output for that minterm.

	00	01	11	10
	$\overline{B} \cdot \overline{C}$	$\overline{B} \cdot C$	$B \cdot C$	$B \cdot \overline{C}$
\overline{A}	0	0	1	0
A	1	0	1	1

Karnaugh maps

- Karnaugh maps can be of any size, and have any number of inputs.
 - ▣ 4 inputs here

		00	01	11	10
		$\bar{C} \cdot \bar{D}$	$\bar{C} \cdot D$	$C \cdot D$	$C \cdot \bar{D}$
00	$\bar{A} \cdot \bar{B}$	m_0	m_1	m_3	m_2
01	$\bar{A} \cdot B$	m_4	m_5	m_7	m_6
11	$A \cdot B$	m_{12}	m_{13}	m_{15}	m_{14}
10	$A \cdot \bar{B}$	m_8	m_9	m_{11}	m_{10}

- Once again, remember the trick to guarantee adjacent terms differ by one input:
00 01 11 10

Karnaugh maps

- Since **adjacent minterms only differ by a single input**, they can be grouped into a single term that omits that input.


Example:

$$Y = m_{15} + m_{14}$$

$$= A \cdot B \cdot C \cdot D + A \cdot B \cdot C \cdot \bar{D}$$

$$= A \cdot B \cdot C \cdot (D + \bar{D})$$

$$= A \cdot B \cdot C$$

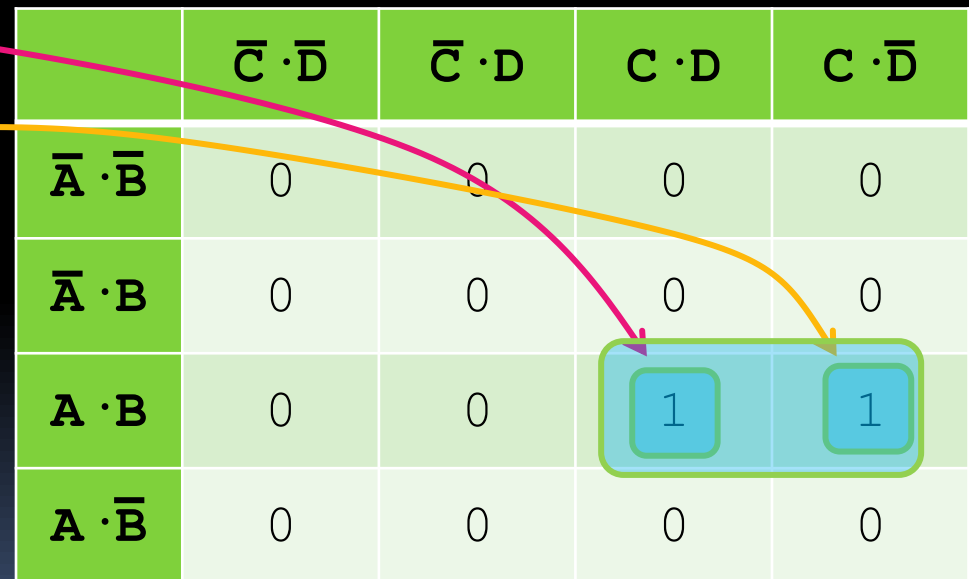

	$\bar{C} \cdot \bar{D}$	$\bar{C} \cdot D$	$C \cdot D$	$C \cdot \bar{D}$
$\bar{A} \cdot \bar{B}$	0	0	0	0
$\bar{A} \cdot B$	0	0	0	0
$A \cdot B$	0	0	1	1
$A \cdot \bar{B}$	0	0	0	0

Using Karnaugh maps

- Once Karnaugh maps are created, draw boxes **over groups of high output values**.
 - Boxes must **cover all ones** and **cannot cover any zero**.
 - Boxes must be **rectangular, and aligned** with map.
 - Size of each box (number of values it contains) must be a **power of 2**. (1,2,4,8,16,...)
 - Boxes **may overlap** with each other.
 - Boxes **may wrap across edges** of map.

	$\overline{B} \cdot \overline{C}$	$\overline{B} \cdot C$	$B \cdot C$	$B \cdot \overline{C}$
\overline{A}	0	0	1	0
A	1	0	1	1

	$\overline{B} \cdot \overline{C}$	$\overline{B} \cdot C$	$B \cdot C$	$B \cdot \overline{C}$
\overline{A}	0	1	1	0
A	0	0	1	0



Must be rectangle!

	$\overline{B} \cdot \overline{C}$	$\overline{B} \cdot C$	$B \cdot C$	$B \cdot \overline{C}$
\overline{A}	0	1	1	0
A	0	0	1	0



Two boxes
overlapping each
other is fine.

	$\overline{B} \cdot \overline{C}$	$\overline{B} \cdot C$	$B \cdot C$	$B \cdot \overline{C}$
\overline{A}	0	1	1	1
A	0	0	0	0



Number of values
contained in each grouping
must be power of 2.

	$\overline{B} \cdot \overline{C}$	$\overline{B} \cdot C$	$B \cdot C$	$B \cdot \overline{C}$
\overline{A}	0	1	1	1
A	0	0	0	0



1 is a power of 2

$$1 = 2^0$$

	$\overline{B} \cdot \overline{C}$	$\overline{B} \cdot C$	$B \cdot C$	$B \cdot \overline{C}$
\overline{A}	0	1	1	0
A	0	1	1	0



Rectangle, with
power of 2 entries

	$\overline{B} \cdot \overline{C}$	$\overline{B} \cdot C$	$B \cdot C$	$B \cdot \overline{C}$
\overline{A}	0	1	0	0
A	0	0	1	0



Must be aligned
with map.

	$\overline{B} \cdot \overline{C}$	$\overline{B} \cdot C$	$B \cdot C$	$B \cdot \overline{C}$
\overline{A}	0	0	0	0
A	1	0	0	1



Wrapping across
edge is fine.

So... how to find smallest expression

Cover all the high values (1's) using the **smallest number** of valid groupings that are as **large** as possible.

	$\bar{B} \cdot \bar{C}$	$\bar{B} \cdot C$	$B \cdot C$	$B \cdot \bar{C}$
\bar{A}	0	0	1	0
A	1	0	1	1



	$\bar{B} \cdot \bar{C}$	$\bar{B} \cdot C$	$B \cdot C$	$B \cdot \bar{C}$
\bar{A}	0	0	1	0
A	1	0	1	1

So... how to find smallest expression

Cover all the high values (1's) using the **smallest number** of valid groupings that are as **large** as possible.

	$\bar{B} \cdot \bar{C}$	$\bar{B} \cdot C$	$B \cdot C$	$B \cdot \bar{C}$
\bar{A}	0	0	1	0
A	1	0	1	1



	$\bar{B} \cdot \bar{C}$	$\bar{B} \cdot C$	$B \cdot C$	$B \cdot \bar{C}$
\bar{A}	0	0	1	0
A	1	0	1	1

	$\bar{B} \cdot \bar{C}$	$\bar{B} \cdot C$	$B \cdot C$	$B \cdot \bar{C}$
\bar{A}	0	1	1	1
A	0	0	1	1




	$\bar{B} \cdot \bar{C}$	$\bar{B} \cdot C$	$B \cdot C$	$B \cdot \bar{C}$
\bar{A}	0	1	1	1
A	0	0	1	1

Using Karnaugh maps

	$\overline{B} \cdot \overline{C}$	$\overline{B} \cdot C$	$B \cdot C$	$B \cdot \overline{C}$
\overline{A}	0	0	1	0
A	1	0	1	1

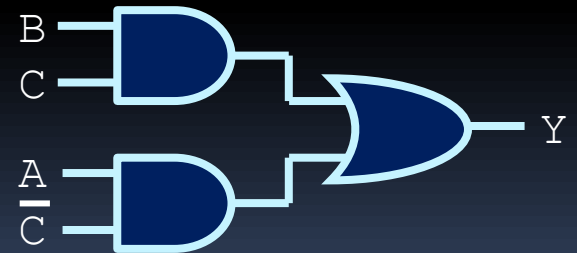- Once you find the minimal number of boxes that cover all the high outputs, create Boolean expressions from the inputs that are common to all elements in the box.
- For this example:
 - Vertical box: $B \cdot C$
 - Horizontal box: $A \cdot \overline{C}$
 - Overall equation: $Y = B \cdot C + A \cdot \overline{C}$



Karnaugh maps and maxterms

- Can also use this technique to group maxterms together as well.

- Karnaugh maps with **maxterms** involves **grouping the zero entries** together, instead of grouping the entries with one values.

	$C+D$	$C+\bar{D}$	$\bar{C}+\bar{D}$	$\bar{C}+D$
$A+B$	M_0	M_1	M_3	M_2
$A+\bar{B}$	M_4	M_5	M_7	M_6
$\bar{A}+\bar{B}$	M_{12}	M_{13}	M_{15}	M_{14}
$\bar{A}+B$	M_8	M_9	M_{11}	M_{10}

Quick Exercise

$$Y = \overline{A} \cdot \overline{B} \cdot C \cdot \overline{D} + \overline{A} \cdot B \cdot \overline{C} \cdot \overline{D} + \overline{A} \cdot B \cdot \overline{C} \cdot D + A \cdot B \cdot \overline{C} \cdot \overline{D} + A \cdot B \cdot \overline{C} \cdot D + A \cdot \overline{B} \cdot C \cdot \overline{D}$$

	$\overline{C} \cdot \overline{D}$	$\overline{C} \cdot D$	$C \cdot D$	$C \cdot \overline{D}$
$\overline{A} \cdot \overline{B}$	0	0	0	1
$\overline{A} \cdot B$	1	1	0	0
$A \cdot B$	1	1	0	0
$A \cdot \overline{B}$	0	0	0	1

- $B\overline{C} + \overline{B}C\overline{D}$

Circuit Creation Algorithm

- Understand desired behaviour
- Write truth table
- Write SOM (or POM) for truth table
- Simplify SOM using K-Map
- Translate simplified SOM into Circuits
- Celebrate!