 


Week 4, Part E:

Flip flops





Reminder

- We are trying to a circuit that can store a bit.
- NAND / NOR feedback – oscillation.
- SR latches – no clock.
- Clocked SR latches – forbidden state.
- D latches – have clocks, no forbidden state.
 - But timing issues.




Fixing latch timing issues

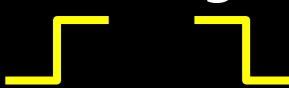 - Preferable behaviour:
 - ▣ Have output change only once when the clock changes. 
- Solution: create **disconnect between circuit output and circuit input**, to prevent unwanted feedback and changes to output.





SR master-slave flip-flop

 - A **flip-flop** is a latched circuit whose output is triggered with the **rising edge** or **falling edge** of a clock pulse.
- Example: the SR master-slave flip-flop



SR master-slave flip-flop

 
 


propa-
gation
delay




Flip flop Behaviour Summary

  - For input to propagate to output, it takes each of the latches to be active once.
- First latch changes on “flip”.
- Output can only change upon “flop”, which is basically the falling edge of the clock signal
- At most one change per clock cycle





Edge-triggered D flip-flop

 - SR flip-flops still have issues of unstable behaviour (race condition) when $S=1$ $R=1$
- Solution: **D flip-flop**
 - Connect D latch to the input of a SR latch.
 - **Negative-edge triggered** flip-flop (like the SR)





Flip-flop behaviour

  - Observe the behaviour:
 - ▣ If the clock signal is high, the input to the first latch is sent out to the second.
 - ▣ The second latch doesn't do anything until the clock signal goes down again.
 - ▣ When it clock goes from high to low, the first latch stops transmitting a signal, and the second one starts.




Flip-flop behaviour

  - Continued from previous:
 - If the input to D changes, the change isn't transmitted to the second latch until the clock goes high again.
 - Once the clock goes high, the first latch starts transmitting at the same time as the second latch stops.



Edge-triggered flip-flop

 - Alternative: **positive-edge triggered** flip-flops





- These are the most commonly-used flip-flop circuits (and our choice for the course).
 - When we say just “flip-flop”, we usually mean this.






Notation



- Latches

  

- Clocked latches

  
 


- Edge-triggered flip-flops

  

Other Flip-Flops

  - The **T flip-flop**:
 - Like the D flip-flop, except that it **toggles** its value whenever the input to T is high.




Other Flip-Flops

- The **JK Flip-Flop**:


- Takes advantage of all combinations of two inputs (J & K) to produce four different behaviours:

 - if J and K are 0, maintain output.
- if J is 0 and K is 1, set output to 0.
- if J is 1 and K is 0, set output to 1.
- if J and K are 1, toggle output value.



Sequential circuit design

 - Similar to creating combinational circuits, with extra considerations:
 - The flip-flops now provide extra inputs to the circuit
 - Extra circuitry needs to be designed for the flip-flop inputs.
 - ...which is next week's lecture 😊



Today we learned

- Sequential circuits – circuits with memory
- Latch
- Flip-flop

Next week

- Registers, Counters
- Finite State Machines
- Sequential circuit design

