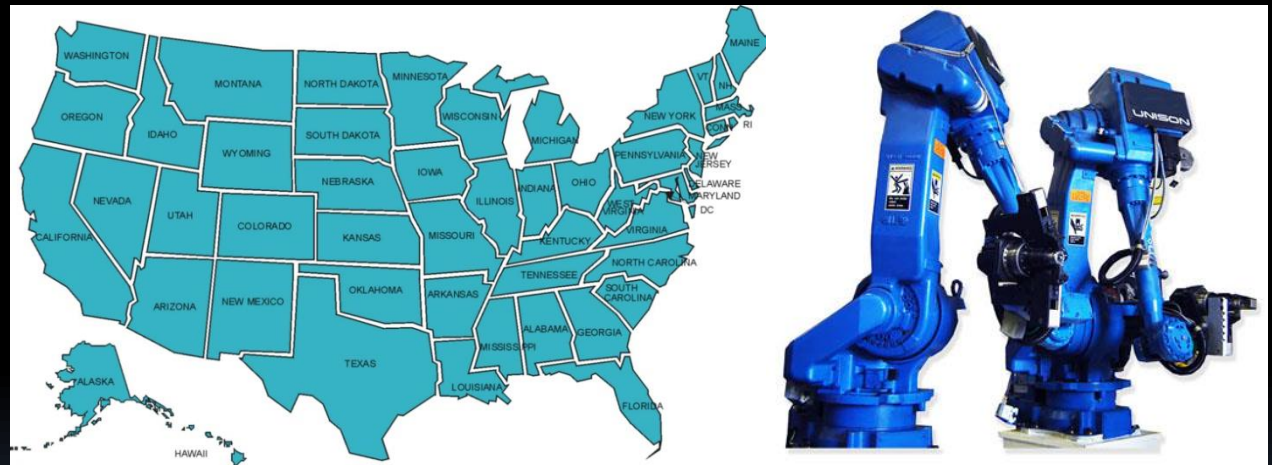


Week 5, part C: State Machines




Reminder

- Sequential circuits are the basis for memory, instruction processing, and any other operation that requires the circuit to **remember past data values**.
- Our memory of the past is called the **state** of the circuit.



Designing with flip-flops

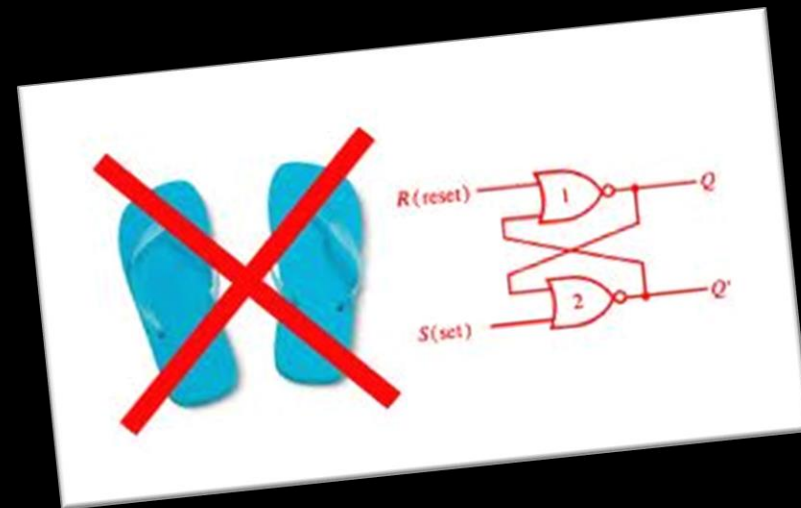- We can use flip-flops to store bits of state for sequential circuits.




- But how do you **design** these circuits?



Designing with flip-flops


- Sequential circuits use combinational logic to determine what the next state of the system should be, based on the past state and the current input values:

input + previous state → next state

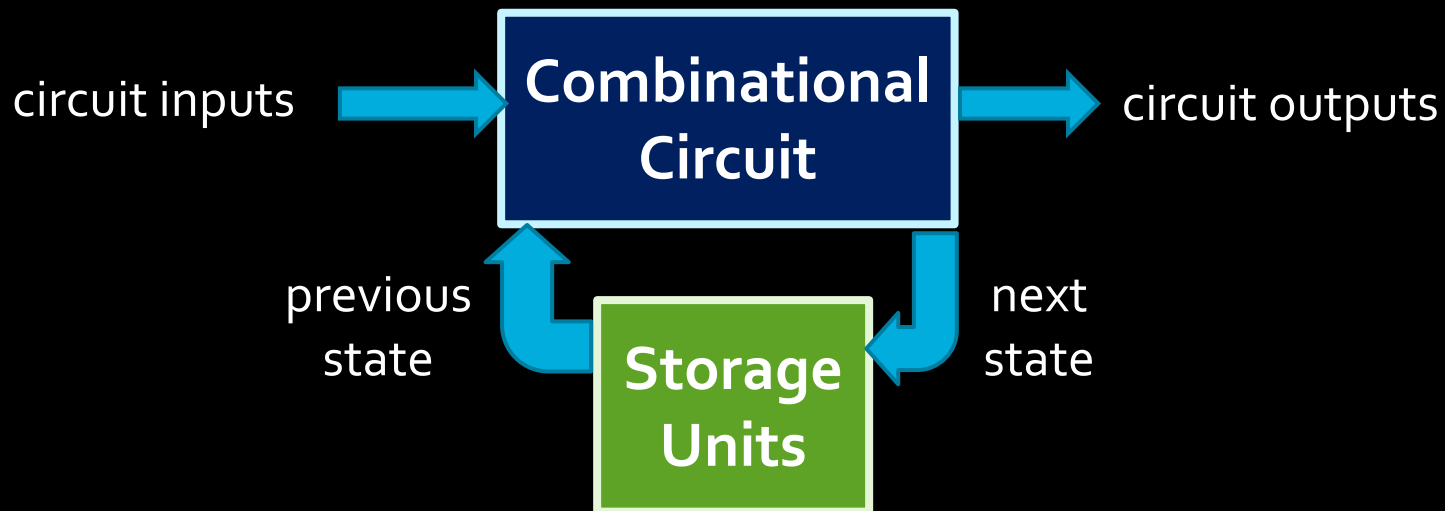

State example: Counters

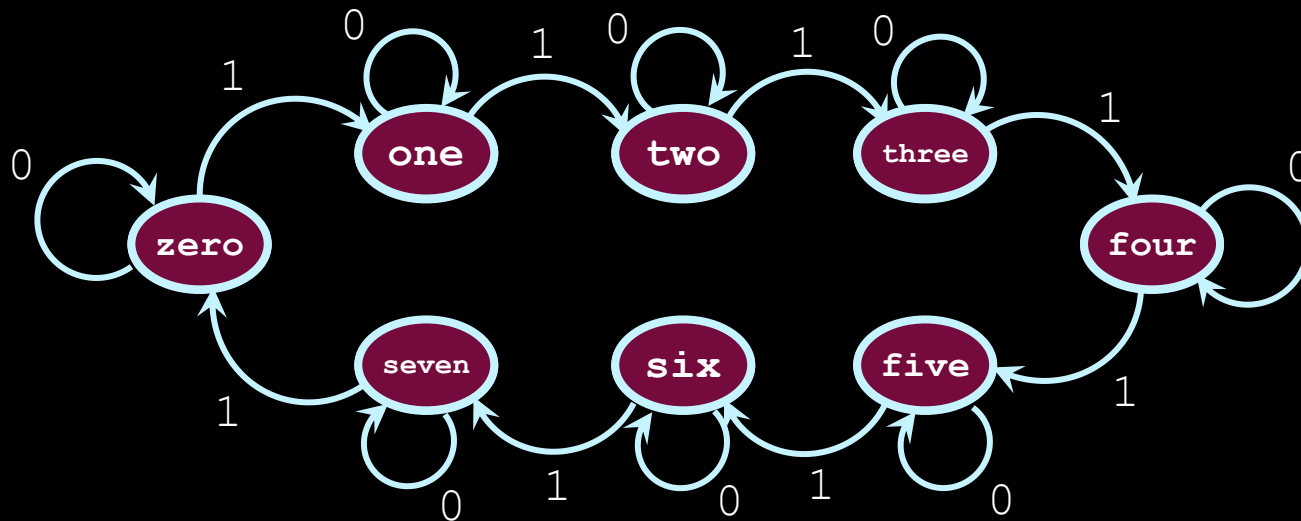- With counters, each state is the current number that is stored in the counter.



- On each clock tick, the circuit **transitions** from one state to the next, based on the inputs.



State Tables

- State tables help to illustrate how the states of the circuit change with various input values.
 - Transitions are understood to take place on the clock ticks
 - (e.g., rising edge)

prev

State	Write	State
zero	0	zero
zero	1	one
one	0	one
one	1	two
two	0	two
two	1	three
three	0	three
three	1	four
four	0	four
four	1	five
five	0	five
five	1	six
six	0	six
six	1	seven
seven	0	seven
seven	1	zero

next



State Tables

- Same table as on the previous slide, but with the actual flip-flop values instead of state labels.
- Note: Flip-flop values are both inputs and outputs of the circuit here.

F ₂	F ₁	F ₀	Write	F ₂	F ₁	F ₀
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	0	0	0	1
0	0	1	1	0	1	0
0	1	0	0	0	1	0
0	1	0	1	0	1	1
0	1	1	0	0	1	1
0	1	1	1	1	0	0
1	0	0	0	1	0	0
1	0	0	1	1	0	1
1	0	1	0	1	0	1
1	0	1	1	1	1	0
1	1	0	0	1	1	0
1	1	0	1	1	1	1
1	1	1	0	1	1	1
1	1	1	1	0	0	0



and this brings us to...

Finite State Machines



Finite State Machines (FSMs)

- From theory courses...
 - A **Finite State Machine** is an abstract model that captures behaviour (e.g., of a sequential circuit).
- A FSM is defined (in general) as:
 - A finite set of **states**,
 - A finite set of **transitions** between states, **triggered by inputs** to the state machine,
 - **Output values** that are associated with each state or each transition (depending on the machine),
 - Start and end states for the state machine.



As seen in other courses...

- You will see (or have seen) finite state machines in other context:
 - Grammars of a language
 - Modeling sequence data.
 - Modeling behaviour.
- In CSCB58, finite state machines are models for an actual circuit design.
 - The states represent internal states of the circuit, which are stored in the flip-flop values.



Example #1: Tickle Me Elmo

- Remember how the Tickle Me Elmo works!




Example #1: Tickle Me Elmo

- Toy reacts differently each time it is squeezed:
 - **First squeeze** → *"Ha ha ha...that tickles."*
 - **Second squeeze** → *"Ha ha ha...oh boy."*
 - **Third squeeze** → *"HA HA HA HA...HA HA HA HA...etc"*
- Questions to ask:
 - What are the inputs?
 - What are the states of this machine?
 - How do you change from one state to the next?
 - Who thought this is a good toy for children!?



Example #1: Tickle Me Elmo

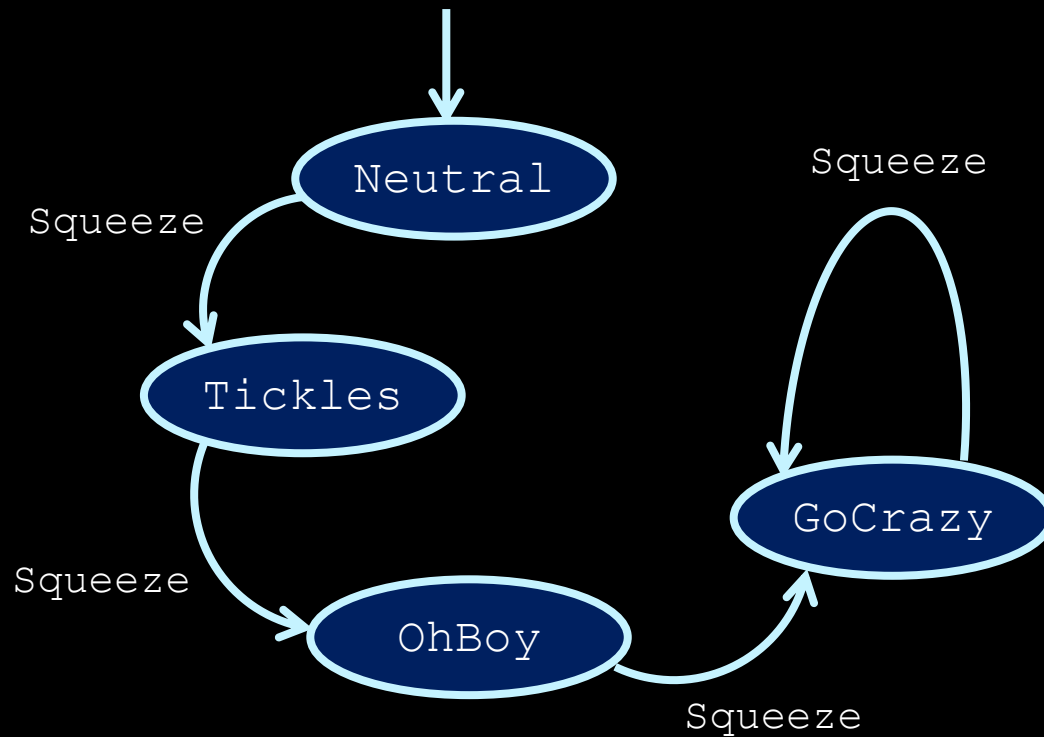

More elaborate FSMs

- Usually our FSM has more than one input, and will trigger a transition based on some input signals but not others.
- Also might have input values that don't cause a transition, but keep the circuit in the same state (transitioning to itself).
 - This is sometimes called **self transition**.



Example #2: Alarm Clock

- Internal state description:
 - Starts in neutral state, until timer signal goes off.
 - Clock moves to alarm state.
 - Alarm state continues until:
 - snooze button is pushed (move to snooze state)
 - alarm is turned off (move to neutral state)
 - timer goes off again (move to neutral state)
 - In snooze state, clock returns to alarm state when the timer signal goes off again.



Let's Draw the State Machine

- Starts in neutral state, until timer signal goes off.
 - Clock moves to alarm state.
- Alarm state continues until one of:
 - snooze button is pushed (move to snooze state)
 - alarm is turned off (move to neutral state)
 - timer goes off again (move to neutral state)
- In snooze state, clock returns to alarm state when the timer signal goes off again.



Let's Draw the State Machine

- Starts in neutral state, until timer signal goes off.
 - Clock moves to alarm state.
- Alarm state continues until one of:
 - snooze button is pushed (move to snooze state)
 - alarm is turned off (move to neutral state)
 - timer goes off again (move to neutral state)
- In snooze state, clock returns to alarm state when the timer signal goes off again.

Neutral


alarm

snooze




Let's Draw the State Machine

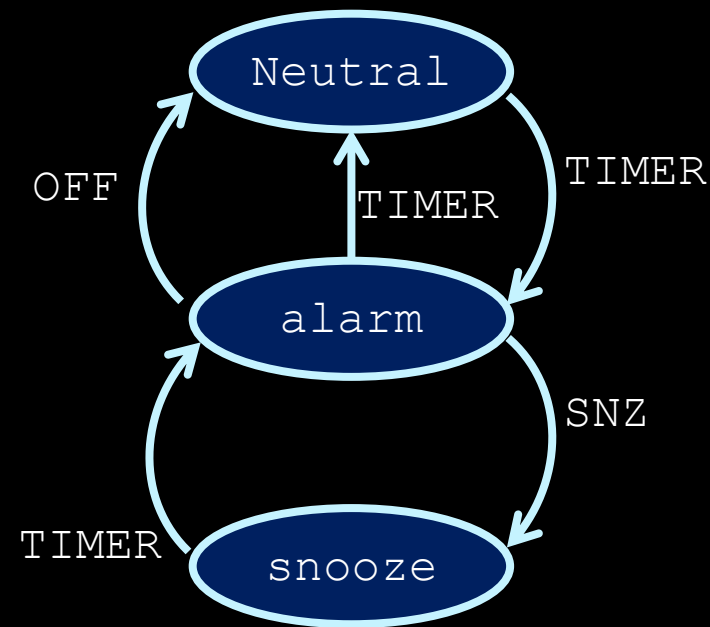- Starts in neutral state, until timer signal goes off.
 - Clock moves to alarm state.
- Alarm state continues until one of:
 - snooze button is pushed (move to snooze state)
 - alarm is turned off (move to neutral state)
 - timer goes off again (move to neutral state)
- In snooze state, clock returns to alarm state when the timer signal goes off again.




Let's Draw the State Machine

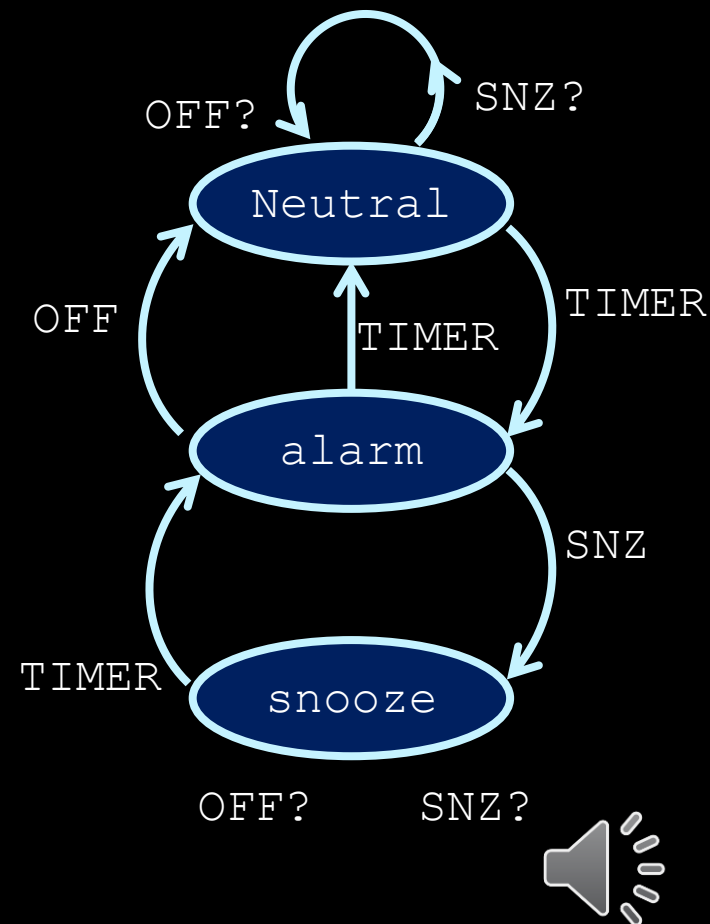- Starts in neutral state, until timer signal goes off.
 - Clock moves to alarm state.
- Alarm state continues until one of:
 - snooze button is pushed (move to snooze state)
 - alarm is turned off (move to neutral state)
 - timer goes off again (move to neutral state)
- In snooze state, clock returns to alarm state when the timer signal goes off again.



Example #3: Traffic Light

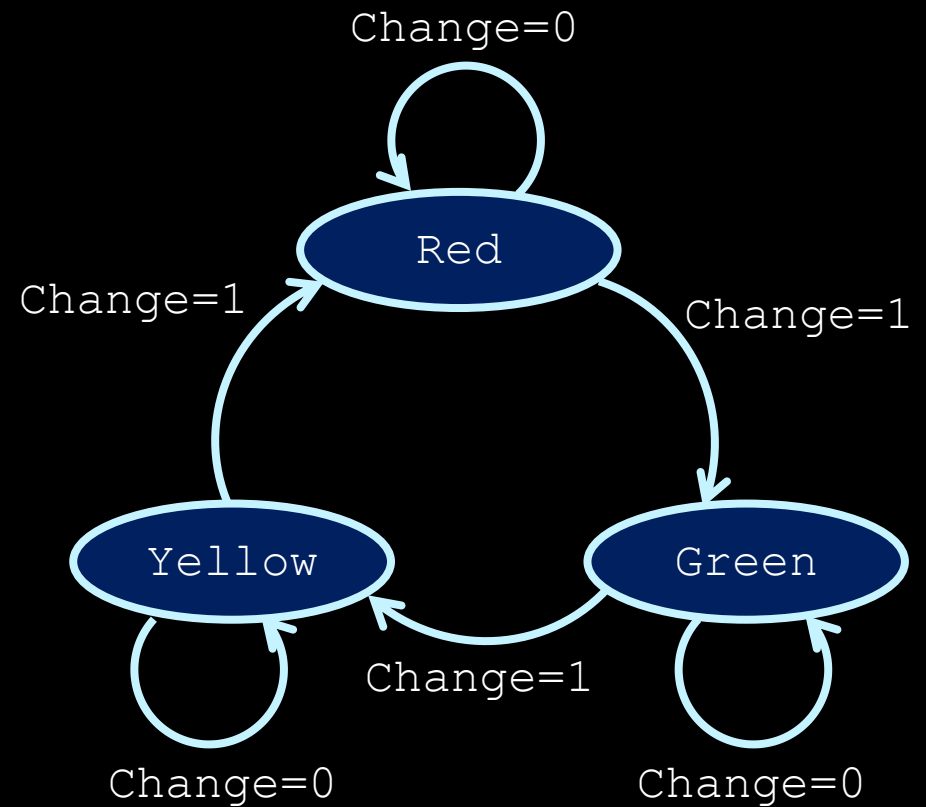

Finite State Machine

- A state machine should be complete including all potential inputs and self transitions.
- OK, so given a story, we can convert it to a state machine (diagram)
- But then what?
 - ▣ Move to next part!

