




# WEEK 4 REVIEW


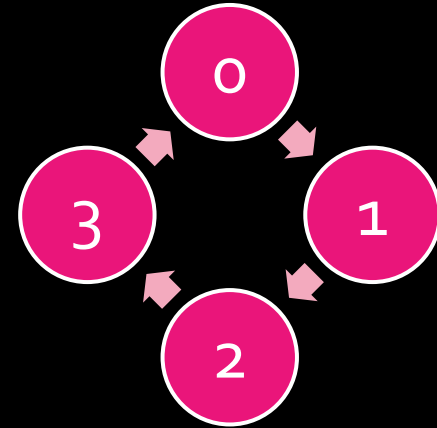
# Sequential Circuits

- How can same input lead to different outputs?
- Sequential logic depends on the **sequence of inputs**, not just current input
- They have some internal **state**




# Creating sequential circuits

Key idea:


split the sequential circuit to two parts.

 - A bunch of flip-flops to store state.
  - This week
- A combinational circuit to handle the logic to manage state and output.
  - More next week.


 
# Feedback for Storing State

- I want to store the output of an AND gate and reuse it as input.




- Does the following work?




- How do we **reason** about this circuit?


# There is a Propagation Delay

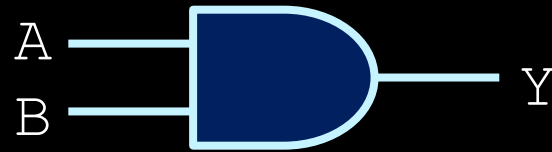

Ideal

 


Considering delays

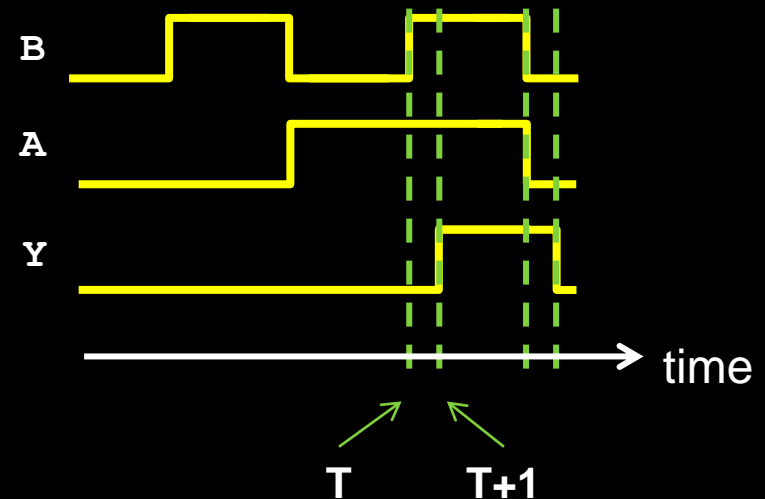

# Feedback Circuit Example (AND)

- Let's analyze it


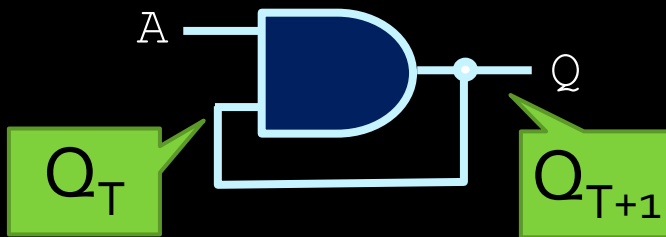


$Q_T$  and  $Q_{T+1}$   
represent the values  
of  $Q$  at a time  $T$ , and  
a point in time  
immediately after  
( $T+1$ )

A	$Q_T$	$Q_{T+1}$
0	0	0
0	1	0
1	0	0
1	1	1
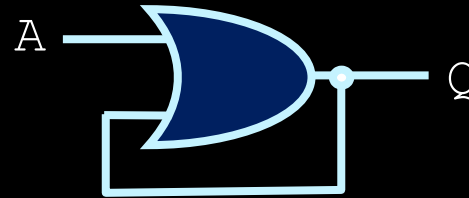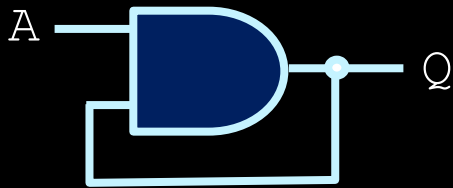
# Feedback Circuit Examples

- Some gates don't have useful results when outputs are fed back on inputs.



Stuck  
at 0


$A$	$Q_T$	$Q_{T+1}$
0	0	0
0	1	0
1	0	0
1	1	1

$A$	$Q_T$	$Q_{T+1}$
0	0	0
0	1	1
1	0	1
1	1	1

Stuck as 1

# Feedback behaviour


- NAND behaviour

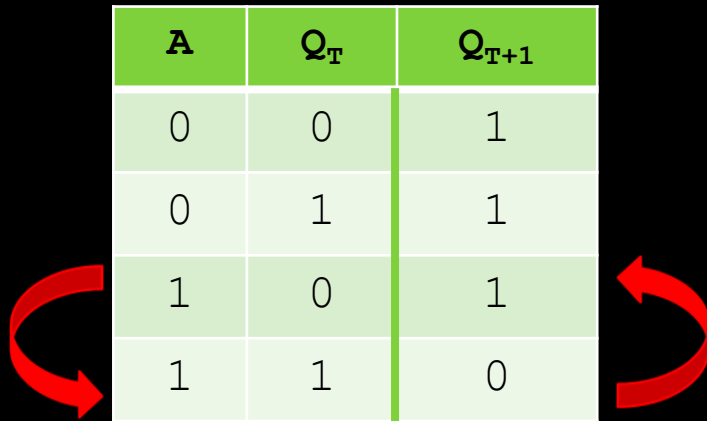

A truth table for NAND behaviour with columns A,  $Q_T$ , and  $Q_{T+1}$ . The table shows that  $Q_{T+1}$  is the logical NOT of A. Red curved arrows on the left and right indicate a feedback loop from  $Q_{T+1}$  back to  $Q_T$ .

A	$Q_T$	$Q_{T+1}$
0	0	1
0	1	1
1	0	1
1	1	0


- NOR behaviour

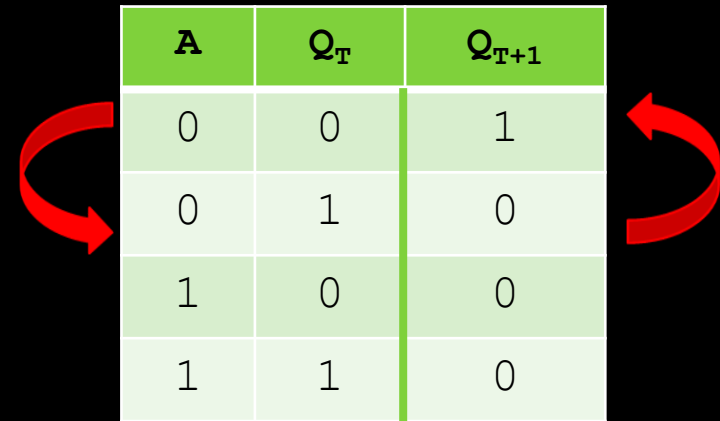

A truth table for NOR behaviour with columns A,  $Q_T$ , and  $Q_{T+1}$ . The table shows that  $Q_{T+1}$  is the logical NOT of (A OR  $Q_T$ ). Red curved arrows on the left and right indicate a feedback loop from  $Q_{T+1}$  back to  $Q_T$ .

A	$Q_T$	$Q_{T+1}$
0	0	1
0	1	0
1	0	0
1	1	0

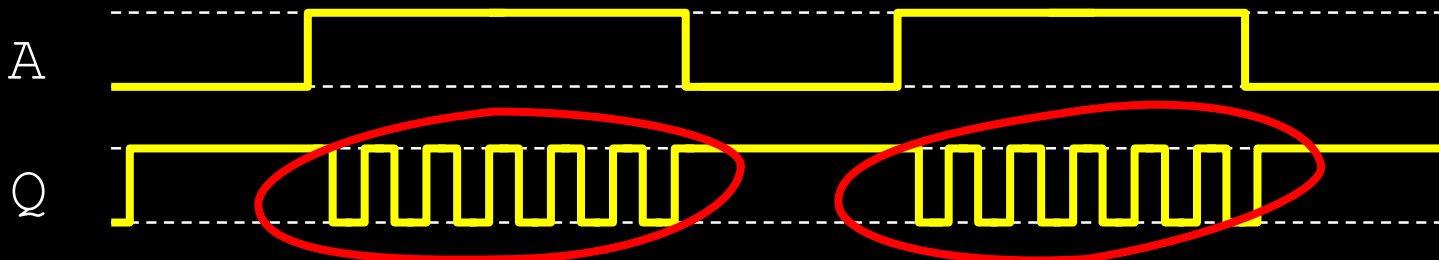
- Output  $Q_{T+1}$  can be changed, based on A.
- They are unstable – **oscillations**.




 
# Question #1


- Is this circuit **stable** or does it **oscillate**?



$Q_T$	$Q_{T+1}$
0	1
1	0
 
## Question #2

- Is this circuit **stable** or does it **oscillate**?




- It **oscillates!**

$Q_T$	$Q_{T+1}$
0	1
1	0

Two red curved arrows are shown. One starts at the bottom-left cell (1, 0) and points to the top-right cell (0, 1). The other starts at the top-right cell (0, 1) and points to the bottom-left cell (1, 0), forming a cycle.
 
## Question #2

- Is this circuit **stable** or does it **oscillate**?




$Q_T$	$A_T$
0	1
1	0

$A_T$	$Q_{T+1}$
1	0
0	1
 
# Question #2

- Is this circuit **stable** or does it **oscillate**?



- It is **stable!**



- $Q=0$  remains 0

$Q_T$	$A_T$
0	1
1	0

$A_T$	$Q_{T+1}$
1	0
0	1



- $Q=1$  remains 1

# Rearrange the circuit...

  
  
# Latches


- We overcome oscillations by combining multiple NAND or NOR gates.



- These circuits are called **latches**.
 
# Question #3

- Complete the truth table
  - ▣ Don't-care inputs **allowed**.
- And name the 4 possible S,R input combinations



S	R	$Q_T$	$\overline{Q}_T$	$Q_{T+1}$	$\overline{Q}_{T+1}$

← Hold


← Reset

← Set

← Forbidden
 
# Question #3

- Complete the truth table
  - ▣ Don't-care inputs **allowed**.
- And name the 4 possible S,R input combinations



S	R	$Q_T$	$\overline{Q}_T$	$Q_{T+1}$	$\overline{Q}_{T+1}$
0	0	0	1	0	1
0	0	1	0	1	0
0	1	X	X	0	1
1	0	X	X	1	0
1	1	X	X	0	0

← Hold

← Reset

← Set

← Forbidden



# Summary: S'R' and SR latches

$\bar{S}\bar{R}$ -latch


$\bar{S}$	$\bar{R}$	$Q_T$	$\bar{Q}_T$	$Q_{T+1}$	$\bar{Q}_{T+1}$
0	0	X	X	1	1
0	1	X	X	1	0
1	0	X	X	0	1
1	1	0	1	0	1
1	1	1	0	1	0

Forbidden state

Set Q to 1

Reset Q to 0

Maintain Q

 

"set" and "reset"  
cannot be both true!

SR-latch


S	R	$Q_T$	$\bar{Q}_T$	$Q_{T+1}$	$\bar{Q}_{T+1}$
0	0	0	1	0	1
0	0	1	0	1	0
0	1	X	X	0	1
1	0	X	X	1	0
1	1	X	X	0	0

Maintain Q

Reset Q to 0


Set Q to 1

Forbidden state

 

 
## Question #4

- Given the input waveforms, sketch the output  $Q$  of an  $\bar{S}\bar{R}$  latch. Assume  $Q$  was zero initially.


 
# Clocks

- A periodic signal that gives timing for our circuit




- **Frequency** = the number of pulses occur per second.



 
# Clocked/Gated latches


- Add a new input C that acts like a “gate” over the inputs:
- If  $C=0$  the latch ignores input
  - Maintains state.
- If  $C=1$  the latch is “active”
  - Responds to input




# Clocked SR latch behaviour

 

C	S	R	$Q_{T+1}$	Result
0	X	X	$Q_T$	hold
1	0	0	$Q_T$	hold
1	0	1	0	Reset
1	1	0	1	Set
<del>1</del>	<del>1</del>	<del>1</del>	?	undefined

 



# D latch

 

- This design is good!
  - ▣ Easy to store a bit: just set D to what you want to store.
  - ▣ Can maintain state as long as C is low
  - ▣ No weird forbidden inputs.

 
 
# D latch is transparent

- Any changes to its inputs are visible to the output when control signal (Clock) is 1.
  - ▣ Output keeps toggling back and forth.
- We want output to change exactly **once per cycle**.


  
# Flip-flops



- Positive edge:  
triggered on rising edge of the clock
- Negative edge:  
triggered on falling edge of the clock





 
 
# Question #6

- Assuming all inputs start low, complete the timing diagram


  
# Flip-flops


- For input to propagate to output, it takes each of the latches to be active once.
- First latch changes on “flip”.
- Output can only change upon “flop”, which is basically the falling edge of the clock signal
- At most one change per clock cycle




# Flip-flops

- We have:
  - D flip-flops (most common type!)
  - SR flip-flops
  - T flip-flops (for “toggle”)
  - JK flip-flops
 
# Week 5: Sequential Circuit Design Part A: registers




# We are here

 
 
# Circuits using flip-flops

- Now that we know about flip-flops and what they do, how do we use them in circuit design?
- What's the benefit in using flip-flops in a circuit at all?




# Example #1: Registers




 
# Registers


- An **n-bit register**: a bank of n flip-flops that share a common clock.
- Registers store a multi-bit value.



- All bits written at the same time.
- Key building block of sequential systems and CPUs.
 
# Shift Registers


- A series of D flip-flops where output of flip-flop  $i$  is connected to input of  $i+1$



- To set the value of an n-bit shift register, shift data into it **one bit at a time**, over n clock cycles.

 
# Shift registers

- Illustration: shifting in 0101010101010101


 
# Shift registers


- Illustration: shifting in 0101010101010101



- After 16 clock cycles....

 
# Load registers

- One can also load a register's values all at once, by feeding signals into each flip-flop:
  - ▣ In this example: a 4-bit **load register**.



 
# Load registers

- **D flip-flop with enable:** controls when the flip-flop is allowed to load D :
  - When  $EN = 1$ ,  $D_2$  is whatever D is → **load D**
  - When  $EN = 0$ ,  $D_2$  is whatever Q is → **maintain Q**



 
# Load registers

- **D flip-flop with enable:** controls when the flip-flop is allowed to load D :
  - When  $EN = 1$ ,  $D_2$  is whatever D is → **load D**
  - When  $EN = 0$ ,  $D_2$  is whatever Q is → **maintain Q**



# Load registers


 


- A register implemented with these new D flip-flops will maintain the old value in the register until overwritten by setting EN high.


  
# Shift vs Load

- Shift registers are **serial** – load bits one at a time
- Load registers are **parallel** – load all bits immediately.
- Load registers (a.k.a “registers”) seem easier to work with... so why?
- Sometimes one wire is better than many.
  - Lack of space on circuit for many wires.
  - Clock skew on long wires, fast clocks.
  - Physics.






# Serial vs Parallel

## PCI

- Parallel
- Many pins

 


## PCIe

- Serial
- Fewer pins... yet faster


 
# Memory Hierarchy

- In computer architecture, registers are the first level in the memory hierarchy.
- The CPU's **most local, fastest storage**
  - 30+ of them on-chip.
- They are the memory units that the CPU interacts with directly for computation.
  - Anything else is too far, and is mediated by registers.
- Higher levels: cache, RAM, disk, etc.




- What else can we build?

# Week 5, part B: Counters




# Idea for A Counter

- Load register + Ripple Carry Adder

 


# Idea for A Counter

- Example: 4-bit counter

 

# Idea for A Counter

- Will this work?


 


- Yes, but lots of gates needed for the adder.



  
# A better idea


- Consider the T flip-flop:
  - ▣ Output is inverted when input T is high.
- What happens when a series of T flip-flops are connected together in sequence?
- More interesting: Connect the *output* of one flip-flop to the **clock** input of the next!



# Counters

 



# Counters

 

- This is a 4-bit **ripple counter**.
- Let's see how it works



# Counters

- Timing diagram

  


# Counters

- Timing diagram

 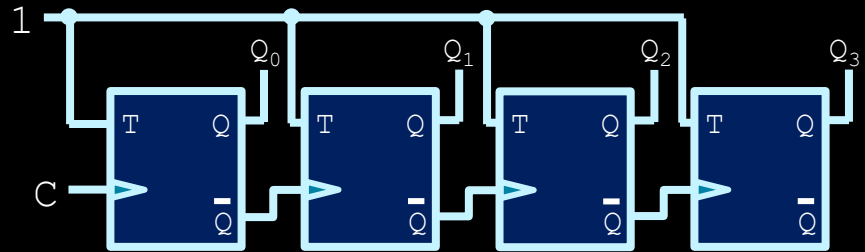

# Counters



- Timing diagram

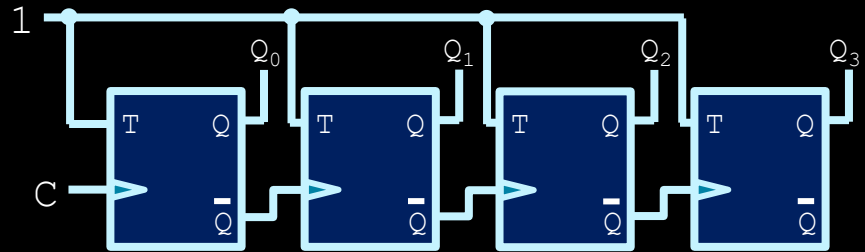[illegible]

  
# Counters

- Timing diagram

- Propagation delay increases for later Qs




# Counters

 

- The **ripple counter**, is an example of an **asynchronous** circuit:  
outputs do not all change with the same clock signal.
- Timing isn't quite synchronized with the rising clock pulse → **hard to know when output is ready**.
  - Cheap to implement, but unreliable for timing.




# Synchronous Counter

 

- This is a **synchronous** counter, with a slight delay.
- Each AND gate combine outputs of **all** previous flip-flops
- Each flip-flop only changes when **all** previous flip flops are set

 
# How it works

- The first FF toggles every clock cycle.
- Every other FF "looks to the left"
  - That's what the AND gates do!
- If **all** FFs to the left are 1 on clock edge, toggle.
  - Like a carry bit generated from adder!
- Otherwise, do not toggle.
- Result:




- 1 1 1 0 → 0 0 0 1 → 1 0 0 1 → 0 1 0 1
- Read from right to left: 0111 → 1000 → 1001

# How it works? Like this

 

[https://www.youtube.com/watch?v=\\_okGZhUE5Do](https://www.youtube.com/watch?v=_okGZhUE5Do)

# Counters with Load

 

When load is high, read from  $R_i$  instead of toggling

only advance when **write** is high (like **T** in T flip-flop)

Counter with **parallel load**, **write**, and **clear** (reset) inputs.

- Useful for countdowns and more.

# What About Custom Designs?

- Registers and counters are simple.
- What about more sophisticated designs?