

Signed subtraction

- Negative numbers are generally stored in 2's complement notation.
 - Reminder: 1's complement \rightarrow bits are the bitwise NOT of the equivalent positive value.
 - 2's complement \rightarrow 1's complement value plus one; results in zero when added to equivalent positive value.
- Subtraction can then be performed by **using the binary adder circuit with negative numbers.**

At the core of subtraction

- Subtraction of a number is simply the addition of its negative value.
- This the negative value is found using the 2's complement process.

- $7 - 3 = 7 + (-3)$

- $-3 - 2 = -3 + (-2)$

Signed Subtraction example

▪ $7 - 3$

$$\begin{array}{r} 0111 \\ -0011 \\ \hline \end{array}$$



$$0111$$

discarded \swarrow

$$\begin{array}{r} +1101 \\ \hline 10100 \end{array}$$



$$0100 = 4_{10}$$

▪ $-3 - 2$

$$\begin{array}{r} 1101 \\ -0010 \\ \hline \end{array}$$



$$1101$$

discarded \swarrow

$$\begin{array}{r} +1110 \\ \hline 11011 \end{array}$$



$$1011 = -5_{10}$$

What about bigger numbers

▪ $53 - 27$

$$\begin{array}{r} 00110101 \\ -00011011 \\ \hline \end{array}$$



$$00110101$$

discarded $+11100101$

$$\begin{array}{r} 100011010 \\ \hline \end{array}$$



$$00011010 = 26_{10}$$

▪ $27 - 53$

$$\begin{array}{r} 00011011 \\ -00110101 \\ \hline \end{array}$$



$$00011011$$

discarded $+11001011$

$$\begin{array}{r} 011100110 \\ \hline \end{array}$$




$$11100110 = -26_{10}$$

Subtraction circuit


- 4-bit subtractor: $X - Y$
 - \rightarrow X plus 2's complement of Y
 - \rightarrow X plus **1's complement of Y** plus **1**

Feed 1 as Carry-In in the least significant FA.

 Use NOT gates to get the 1's complement of Y.



Addition/Subtraction circuit

 

- The full adder circuit can be expanded to incorporate the subtraction operation
 - Remember: 2's complement = 1's complement + 1
 - We connect Sub to Cin

Food for Thought

- What happens if we add these two positive signed binary numbers $0110 + 0011$ (i.e., $6 + 3$)?
 - The result is 1001 .
 - But that is a negative number (-7)! ☹️
- What happens if we add the two negative numbers $1000 + 1111$ (i.e., $-8 + (-1)$)?
 - The result is 0111 with a carry-out. ☹️
- We need to know when the result might be wrong.
 - This is usually indicated in hardware by the **Overflow** flag!
 - More about this when we'll talk about processors.

Subtracting unsigned numbers

- General algorithm for $X - Y$:
(for sign-and-magnitude representation)
 1. Get the 2's complement of the subtrahend Y (the term being subtracted).
 2. Add that value to the minuend X (the term being subtracted from).
 3. If there is an end carry (C_{out} is high), the final result is positive and does not change (set sign bit of output to 0).
 4. If there is no end carry (C_{out} is low), get the 2's complement of the result and set the sign bit of output to 1.

Unsigned subtraction example

- $53 - 27$

$$\begin{array}{r} 00110101 \\ -00011011 \\ \hline \end{array}$$



- $27 - 53$

$$\begin{array}{r} 00011011 \\ -00110101 \\ \hline \end{array}$$



Unsigned subtraction example

▪ $53 - 27$

$$\begin{array}{r} 00110101 \\ -00011011 \\ \hline \end{array}$$



$$\begin{array}{r} 00110101 \\ +11100101 \\ \hline 100011010 \end{array}$$

carry bit
↓
sign bit
is low

00011010

▪ $27 - 53$

$$\begin{array}{r} 00011011 \\ -00110101 \\ \hline \end{array}$$




no carry bit
↓
sign bit
is high

$$\begin{array}{r} 00011011 \\ +11001011 \\ \hline 011100110 \end{array}$$

-00011010

Week 4: Sequential Circuits

Last Week

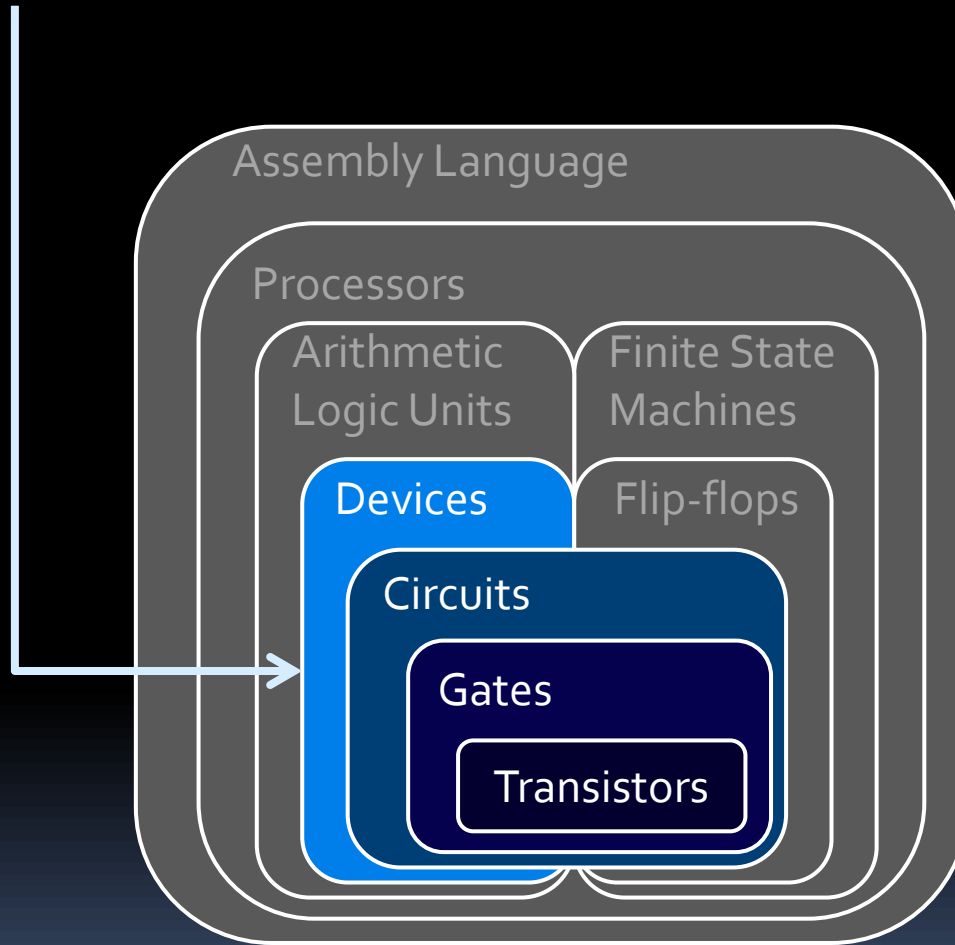

Build A Counter?


- Can you build a device that counts number of key presses?
 - After key is pressed once, hex display should show 1
 - After key is pressed again, show 2
 - Third time: show 3
 - Then reset to 0

Something else to consider..

- Computer specs use terms like “16 GB of RAM” and “5GHz processors”.
 - What do these terms mean?
 - **RAM** = Random Access Memory
 - 16GB = 16 billion chars (bytes)
 - 5 **GHz** = 5 billion clock pulses per second.
 - But what does this mean in circuitry?
 - How do you use circuits to store values?
 - What is the purpose of a clock signal?



This Week

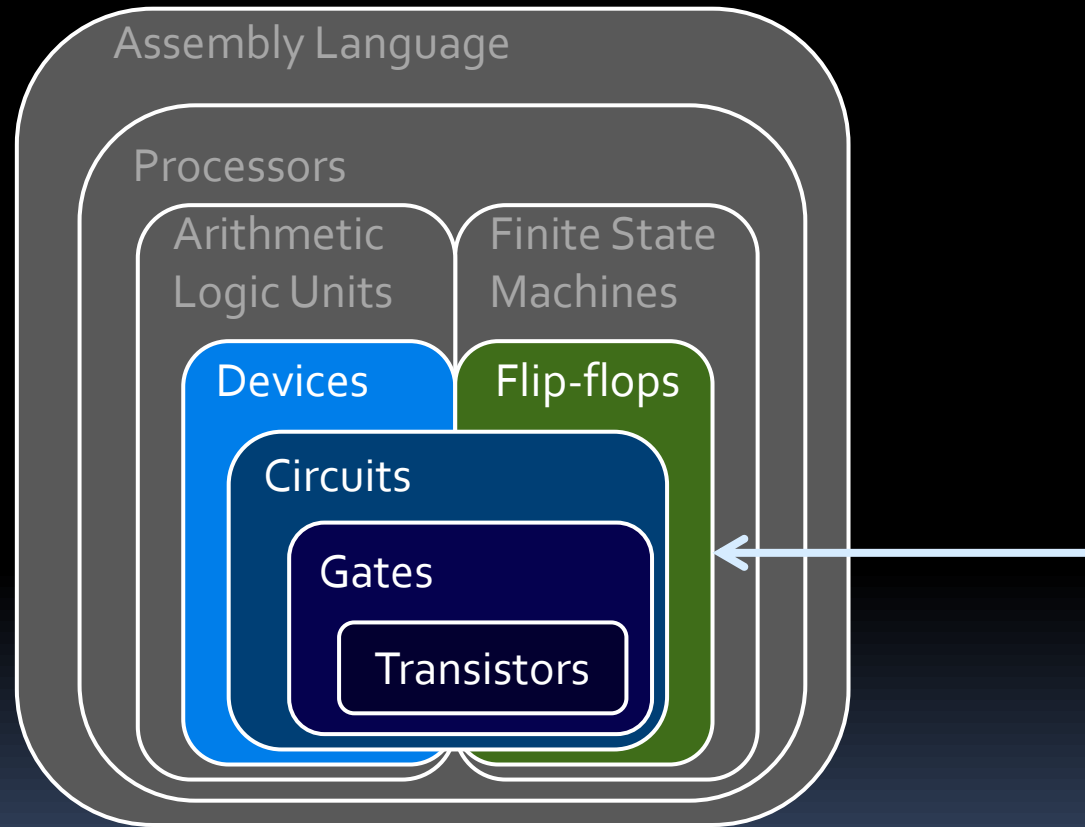


Two kinds of circuits

- So far, we've dealt with **combinational circuits**:
 - Circuits where the output values are entirely dependent and predictable from the input values.
- Another class of circuits: **sequential circuits**
 - Circuits that also depend on both the inputs **and the previous state** of the circuit.



Sequential circuits

 - This creates circuits whose internal state can change over time, where the same input values can result in different outputs.
- Why would we need circuits like this?
 - Memory values
 - Reacting to changing inputs




Creating sequential circuits

  - Essentially, sequential circuits have feedback in the circuit.
 - How is this accomplished?
 - What is the result of having the output of a component or circuit be connected to its input?



Feedback

 


\bar{A}



Storing and Reusing Values

 - I want to store the output of an AND gate and reuse it as input.





- Does the following work?



- How do we reason about this circuit?


Waveform Diagrams

  


Gate Delay

- Outputs don't change instantaneously.
 - Electrons have to move, transistors open/close...
 - Even in combinatorial circuits.
- **Gate Delay** or **Propagation Delay**:
 - “The length of time it takes for an input change to result in the corresponding output change.”


Gate Delays

 

Ideal

 


Considering delays

 

Feedback Circuit Example (AND)

 - Some gates don't have useful results when outputs are fed back on inputs.



Q_T and Q_{T+1} represent the values of Q at a time T, and a point in time immediately after ($T+1$)

A	Q_T	Q_{T+1}
0	0	0
0	1	0
1	0	0
1	1	1


If $A=0$, Q_{T+1} becomes 0 no matter what Q_T was.

What happens next for later values of A?

Q_{T+1} gets stuck at 0 and cannot change ☹️

Feedback Circuit Example (OR)

 - Some gates don't have useful results when outputs are fed back on inputs.



In this truth table, Q_T and Q_{T+1} represent the values of Q at a time T , and a point in time immediately after ($T+1$)

A	Q_T	Q_{T+1}
0	0	0
0	1	1
1	0	1
1	1	1


If $A=1$, Q_{T+1} becomes 1 no matter what Q_T was.

What happens next for later values of A ?

Q_{T+1} gets stuck at 1. Not very useful ☹

Feedback Examples (NAND, NOR)

 
- NAND, NOR gates w/ feedback have more interesting characteristics, which lend themselves to storage devices.



- What makes NAND and NOR feedback circuits different?
 - Unlike the AND and OR gate circuits (which get stuck), the output Q_{T+1} can be changed, based on A .

Feedback Example (NAND)

 - Let's assume we set $A=0$
 - Then, output Q will go to 1.
 - If we leave A unchanged we can store 1 indefinitely!
- If we set $A=1$, Q 's value can change, but there's a catch!




What happens
in these last
two scenarios?

A	Q_T	Q_{T+1}
0	0	1
0	1	1
1	0	1
1	1	0

Unsteady state!
Can't store 0 long!

NAND waveform behaviour

 


A	Q_T	Q_{T+1}
0	0	1
0	1	1
1	0	1
1	1	0



Gate delay. Output does not change instantaneously

Feedback Example (NOR)

 - Let's assume we set $A=1$
- Then, output Q will go to 0.
- If we leave A unchanged we can store 0 indefinitely!
- If we flip A , we can change Q , but there's a catch here too!



A	Q_T	Q_{T+1}
0	0	1
0	1	0
1	0	0
1	1	0

Feedback behaviour

- NAND behaviour


A	Q_T	Q_{T+1}
0	0	1
0	1	1
1	0	1
1	1	0

- NOR behaviour

A	Q_T	Q_{T+1}
0	0	1
0	1	0
1	0	0
1	1	0

- Output Q_{T+1} can be changed, based on A.
- However, gates like these that feed back on themselves enter an **unstable state**.
 - The output is not stable.

NAND waveform behaviour

 


A	Q_T	Q_{T+1}
0	0	1
0	1	1
1	0	1
1	1	0



We want to avoid this. We should be able to store high and low values for as long as we want, and change those values as needed.

Latches


 
- If multiple gates of these types are combined, you can get stable behaviour.



- These circuits are called **latches**.



$\overline{S}\overline{R}$ latch

  - Let's see what happens when the input values are changed...
 - Assume that \overline{S} and \overline{R} are set to 1 and 0 to start.
 - The \overline{R} input sets the output \overline{Q} to 1, which sets the output Q to 0.
 - Setting \overline{R} to 1 keeps the output value \overline{Q} at 1, which maintains both output values.




$\overline{S}\overline{R}$ latch

  - (continuing from previous)
 - ▣ \overline{S} and \overline{R} start with values of 1, when \overline{S} is set to 0.
 - ▣ This sets output Q to 1, which sets the output \overline{Q} to 0.
 - ▣ Setting \overline{S} back to 1 keeps the output value \overline{Q} at 0, which maintains both output values.
- Conclusion: the input 11 maintains the previous output state!




$\overline{S}\overline{R}$ latch

 

\overline{S}	\overline{R}	Q_T	\overline{Q}_T	Q_{T+1}	\overline{Q}_{T+1}
0	0	X	X	1	1
0	1	X	X	1	0
1	0	X	X	0	1
1	1	0	1	0	1
1	1	1	0	1	0

- \overline{S} and \overline{R} are called “set” and “reset” respectively.
- Note how the circuit “remembers” its signal when going from 10 or 01 to 11.
- Going from 00 to 11 produces unstable behaviour!
 - In the sense that we don’t know what the output will be. It can be 0 or 1, depending on which input changes first.

SR latch


 


S	R	Q_T	\bar{Q}_T	Q_{T+1}	\bar{Q}_{T+1}
0	0	0	1	0	1
0	0	1	0	1	0
0	1	X	X	0	1
1	0	X	X	1	0
1	1	X	X	0	0

- In this case, S and R are “set” and “reset”.
- In this case, the circuit “remembers” previous output when going from 10 or 01 to 00.
- As with $\bar{S}\bar{R}$ latch, unstable behaviour is possible, but this time when inputs go from 11 to 00.

SR latch timing diagram

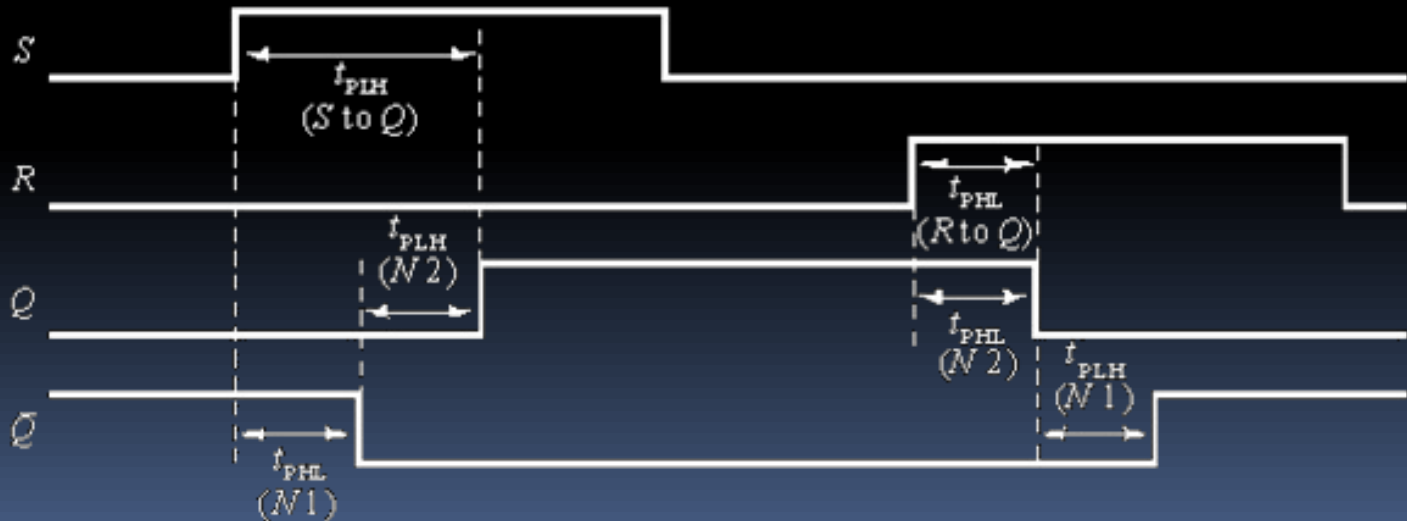 - Important to note that the output signals don't change instantaneously.



More on instability


- Unstable behaviour occurs when a $\overline{S}\overline{R}$ latch goes from 00 to 11, or a SR latch goes from 11 to 00.
 - The signals don't change simultaneously, so the outcome depends on which signal changes first.
- Because of the unstable behaviour, 00 is considered a **forbidden state** in NAND-based $\overline{S}\overline{R}$ latches, and 11 is considered a forbidden state in NOR-based SR latches.

Reading from latches


- Now we have circuit units that can store high or low values. When can we read from them?
 - For instance, when do we know when the output is ready to be sampled?
 - If the output is high, how can we tell the difference between a single high value and two high values in a row?
- Need some sort of timing signal, to let the circuit know when the output may be sampled.
 - clock signals.

Clock signals

 - “Clocks” are a regular pulse signal, where the high value indicates that the output of the latch may be sampled.
- Usually drawn as:




- But looks more like:

 


Signal restrictions

 - What's the limit to how fast the latch circuit can be sampled?
- Determined by:
 - latency time of transistors
 - Setup and hold time
 - setup time for clock signal
 - Jitter
 - Gibbs phenomenon
- **Frequency** = how many pulses occur per second, measured in Hertz (or Hz).




Clocked SR latch

 

- Adding another layer of NAND gates to the $\bar{S}\bar{R}$ latch gives us a **clocked SR latch** (or **gated SR latch**)
 - Basically, a latch with a control input signal C.
- The input C is often connected to a pulse signal that alternates regularly between 0 and 1 (clock)


Clocked SR latch behaviour

 - Same behaviour as SR latch, but with timing:
 - ▣ Start off with $S=0$ and $R=1$, like earlier example.
 - ▣ If clock is high, the first NAND gates invert those values, which get inverted again in the output.
 - ▣ Setting both inputs to 0 maintains the output values.




Clocked SR latch behaviour

 - Continued from previous:
 - Now set the clock low.
 - Even if the inputs change, the low clock input prevents the change from reaching the second stage of NAND gates.
 - Result: the clock needs to be high in order for the inputs to have any effect.




Clocked SR latch

 

- This is the typical symbol for a clocked SR latch.
- **This only allows the S and R signals to affect the circuit when the clock input (C) is high.**
- Note: the small NOT circle after the \bar{Q} output is simply the notation to use to denote the inverted output value. It's not an extra NOT gate.


Clocked SR latch behaviour

 

Q_T	S	R	Q_{T+1}	Result
0	0	0	0	no change
0	0	1	0	reset
0	1	0	1	set
0	1	1	?	???
1	0	0	1	no change
1	0	1	0	reset
1	1	0	1	set
1	1	1	?	???

- Wait!
- Where's the clock?
- There's a better way to look at this....


Clocked SR latch behaviour

 

C	S	R	Q_{T+1}	Result
0	X	X	Q_T	no change
1	0	0	Q_T	no change
1	0	1	0	reset
1	1	0	1	set
1	1	1	?	Undefined

- Assuming the clock is 1, we still have a problem when S and R are both 1, since the state of Q is indeterminate.
 - Better design: prevent S and R from both going high.


D latch

 

Q_T	D	Q_{T+1}
0	0	0
0	1	1
1	0	0
1	1	1

- By making the inputs to R and S dependent on a single signal D , you avoid the indeterminate state problem.
- The value of D now sets output Q low or high whenever C is high.


D latch

 

- This design is good, but still has problems.
 - i.e. **timing issues**.
 - How can we maintain state?

Latch timing issues

 - Consider the circuit on the right:
- When the clock signal is high, the output looks like the waveform below:




- Output keeps toggling back and forth.




...what happens next?

Latch timing issues

 - Consider the circuit on the right:
- When the clock signal is high, the output looks like the waveform below:



- Output keeps toggling back and forth.

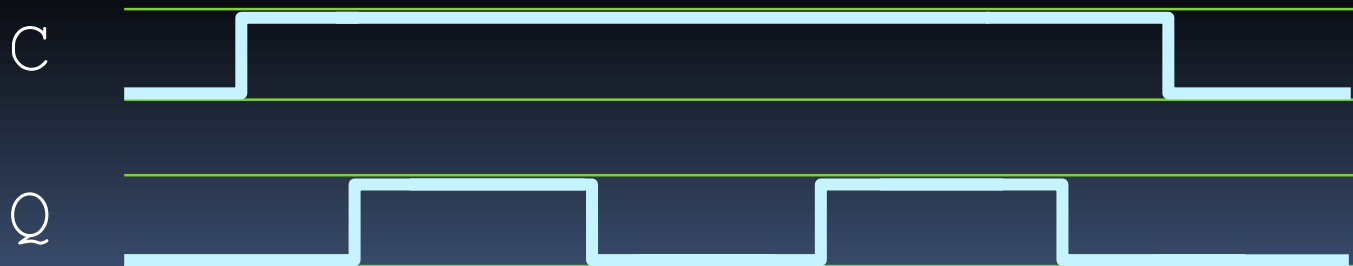

D-Latch is transparent!

- **Transparent** means that
 - Any changes to its inputs are visible to the output when control signal (Clock) is 1.
- **Key Take-away:** The “output of a latch **should not** be applied directly or through combinational logic to the input of the same or another latch when they all have the same control (clock) signal.”